

**CSCE 230, Fall 2013**

**Chapter 5: Basic Processing Unit**


**Part 1: Fundamental Concepts and  
Datapath Design**

Mehmet Can Vuran, Instructor

 University of Nebraska-Lincoln

Acknowledgement: Overheads adapted from those provided by the authors of the textbook

# Hardware Implementation of $A = B + C$

 


- Common clock
- Operation takes one clock cycle.
- Clock period\*  $\geq$   
Propagation\_Delay(A or B) +  
Propagation\_Delay(ALU) +  
Setup\_Time(C)

$$\Leftrightarrow D_{(A \text{ or } B)} + D_{ALU} + D_{setup(C)}$$

\*This computation ignores wire delays which can be quite significant, especially, in FPGA implementations

 
# Generalization to Composition of Combinational-Logic Functions



$$\text{Clock Period} \geq D_{(REG)} + D_F + D_G + D_H + D_{setup(REG)}$$
 
# Pipelining computations

Add buffers between stages to achieve independence.




$$\text{Clock Period} \geq D_{(REG)} + \text{Max}(D_F, D_G, D_H) + D_{setup(REG)}$$

Again, ignoring wire delays


# A note on processor of Chapter 5

- The design uses inter-stage buffers
- Motivation:
  - Easier-to-understand control
  - Easier to generalize to pipelined implementation in Chapter 6

# Computer Architecture

 


# CPU + memory Abstraction

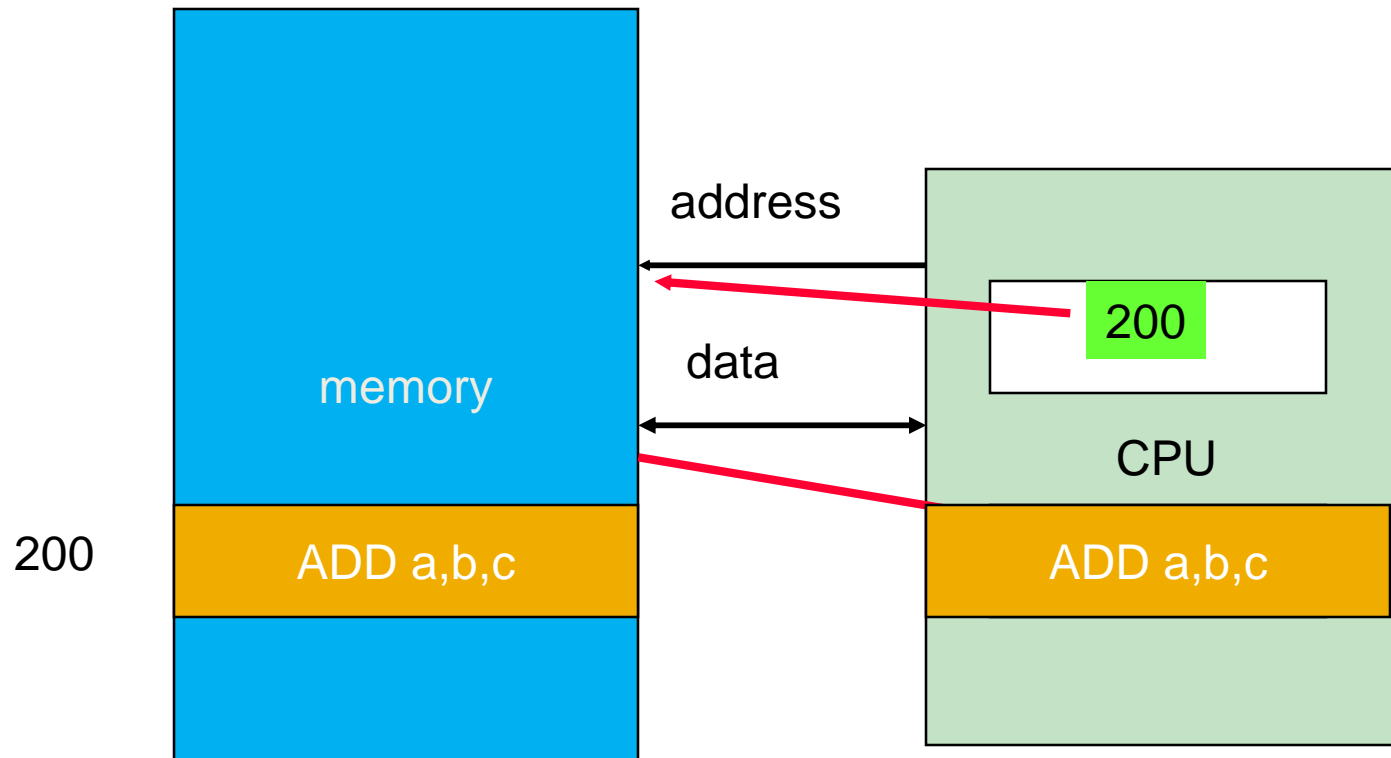
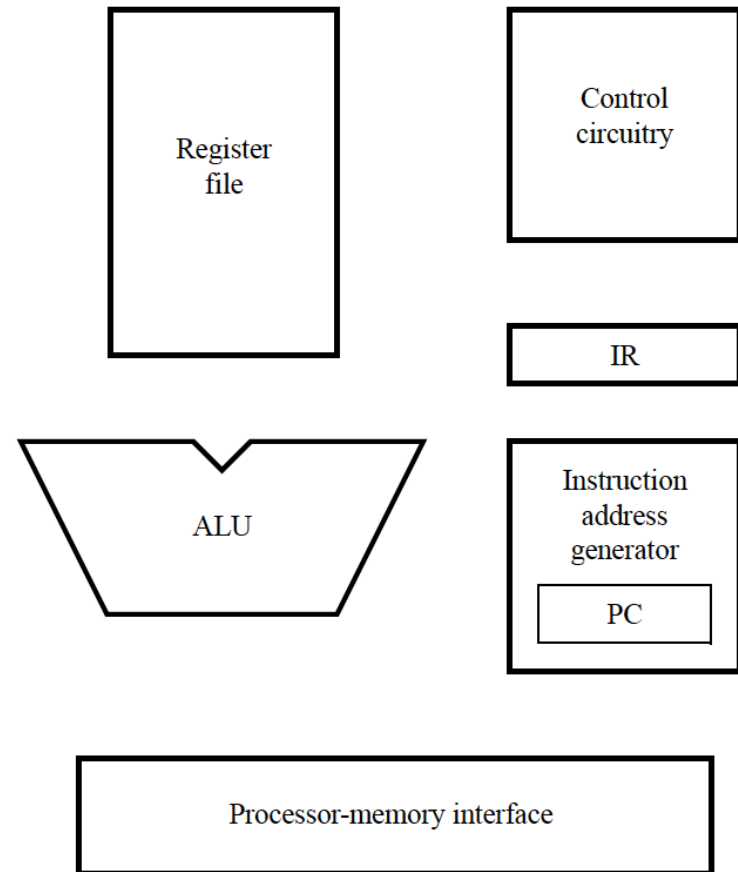
# Processor's main building blocks

- PC provides instruction address.
- Instruction is fetched into IR
- Instruction address generator updates PC
- Control circuitry interprets instruction and generates control signals to perform the actions needed.







# Datapath and controlpath examples for different instruction types.

# Processor's main building blocks

MAX:	Subtract	SP, SP, #20	
	Store	R1, 16(SP)	Push R1
	Store	R2, 12(SP)	Push R2
	...		...
	Store	R5, (SP)	Push R5
	Load	R3, 24(SP)	
	Load	R5, 20(SP)	
	Move	R2, #1	
Loop:	Add	R5, R5, #4	
	Load	R4, (R5)	
	Branch_if_(R1>=R4)	Skip	
	Move	R1, R4	
Skip:	Add	R2, R2, #1	
	Branch_if_(R3>R2)	Loop	
	Store	R1, 24(SP)	
	Load	R1, 16(SP)	Restore R1
	Load	R2, 12(SP)	Restore R2
	...		...
	Load	R5, (SP)	Restore R5
	Return		

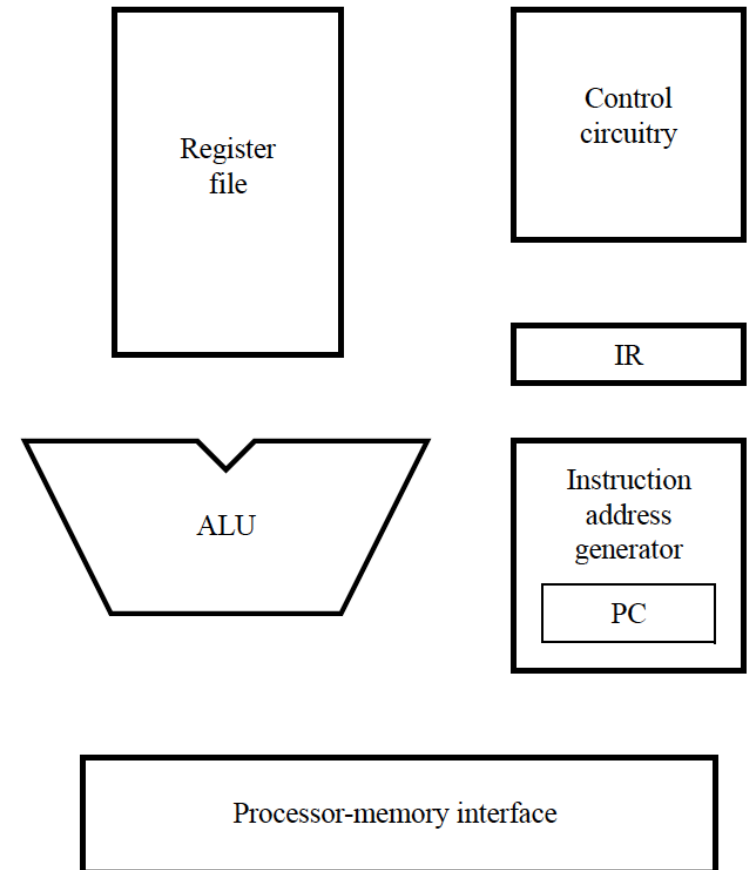

# Processor Loop

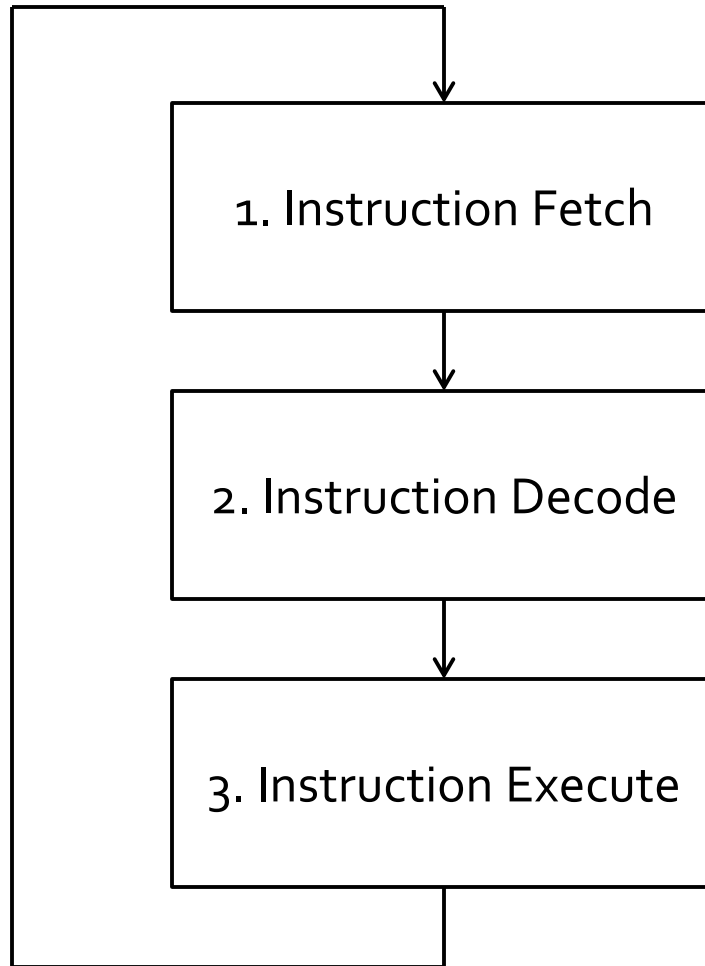

# Instruction Fetch


- Common to all instructions
- (Essential) Read instruction word in memory pointed to by PC into IR
- (Optional) Increment PC (may be overwritten if the next instruction is different)
  - **Important architectural principle:** *Make the common case fast.*

# Instruction Decode

- Common to all instructions
- (Essential) Figure out what the instruction is so that the control signals can be correctly generated for instruction execution.
  - Done by decoding the **instruction opcode field(s)**
- (Optional) Read *source registers* specified in by the register fields of instructions involving register operands.
  - Wasted effort if the instruction does not involve register reads but **this is the common case.**


# Instruction Decode

Add R3, R4, R5

 


(a) Register-operand format

Load R5, X(R7)

 

(b) Immediate-operand format

Branch LOOP

 

(c) Call format

# Instruction Execution

- Depends on *instruction type*.
- *Can be further divided into stages*


# Instruction Execution

- Load R5, X(R7)
- Add R3, R4, R5
- Add R3, R4, #100
- Store R6, X(R8)


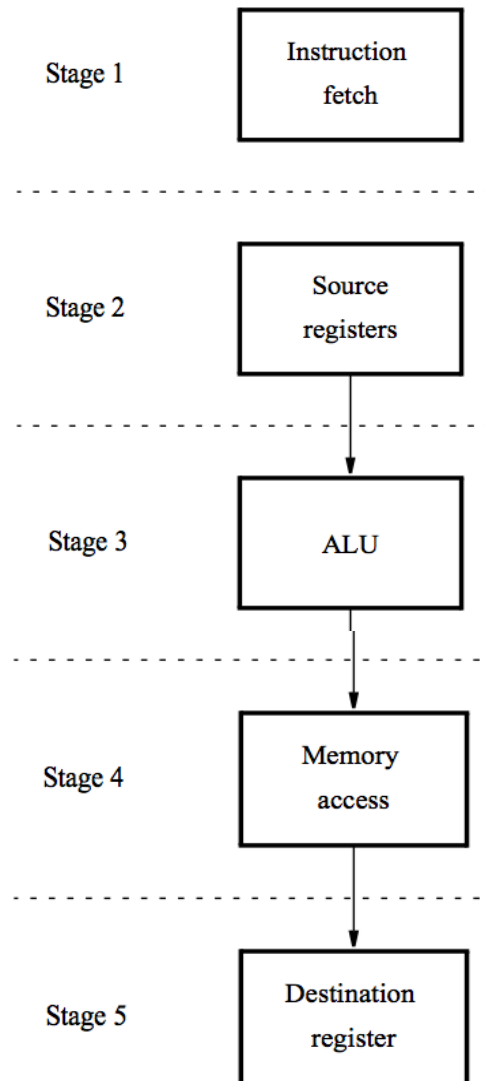
# Five-Stage Execution

- Instruction processing moves from each stage to the next in every clock cycle, after fetch in Stage 1.
- The instruction is decoded and the source registers are read in stage 2.
- Computation takes place in the ALU in stage 3.
- If a memory operation is involved, it takes place in stage 4.
- The result of the instruction is stored in the destination register in stage 5.



# Datapath: Stages 2–5


## 2. Register

## 3. ALU


## 4. Memory
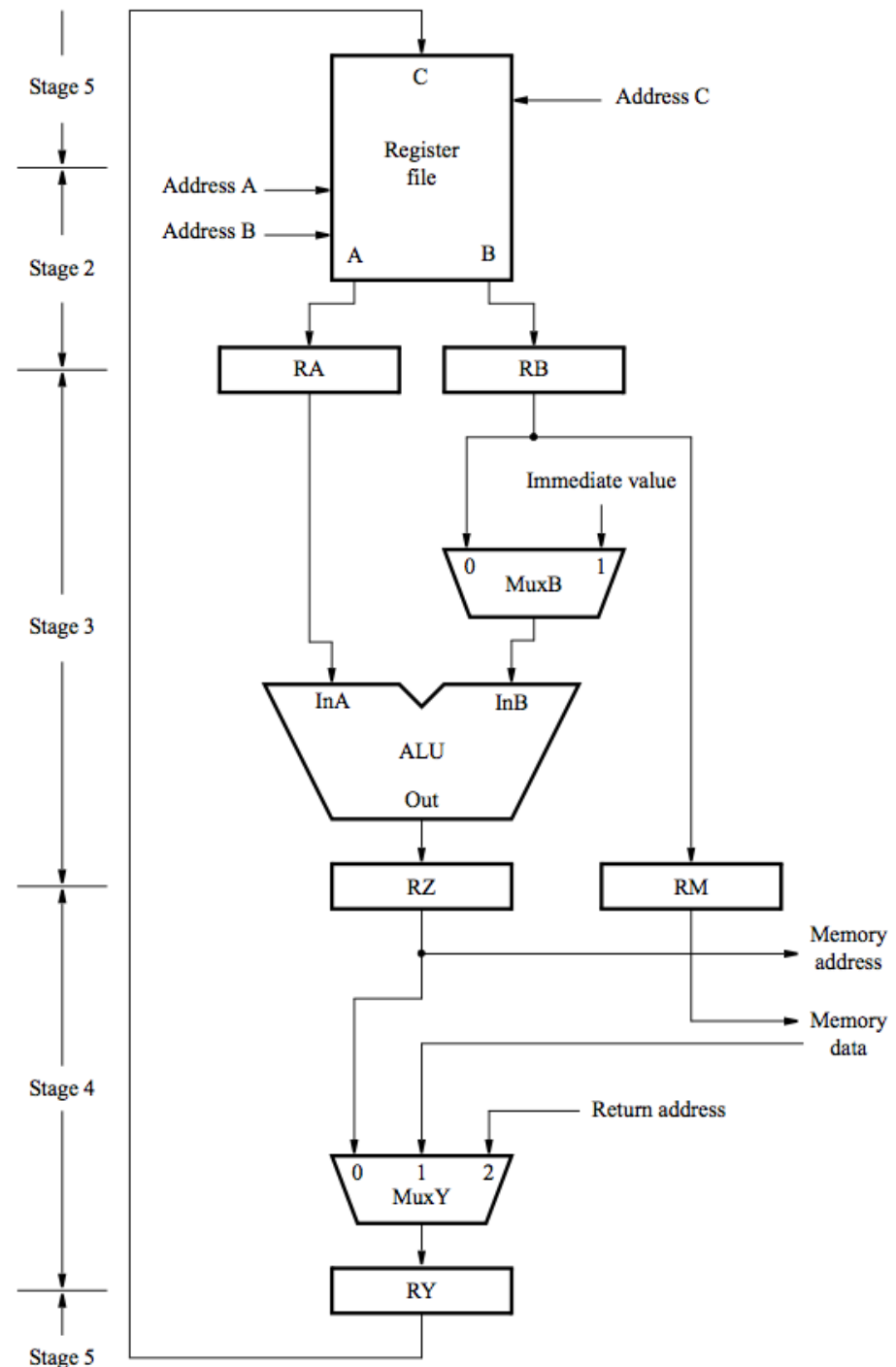
## 5. Writeback


Stage 1  
(Instruction Fetch)  
is shown later.



# Computer Architecture

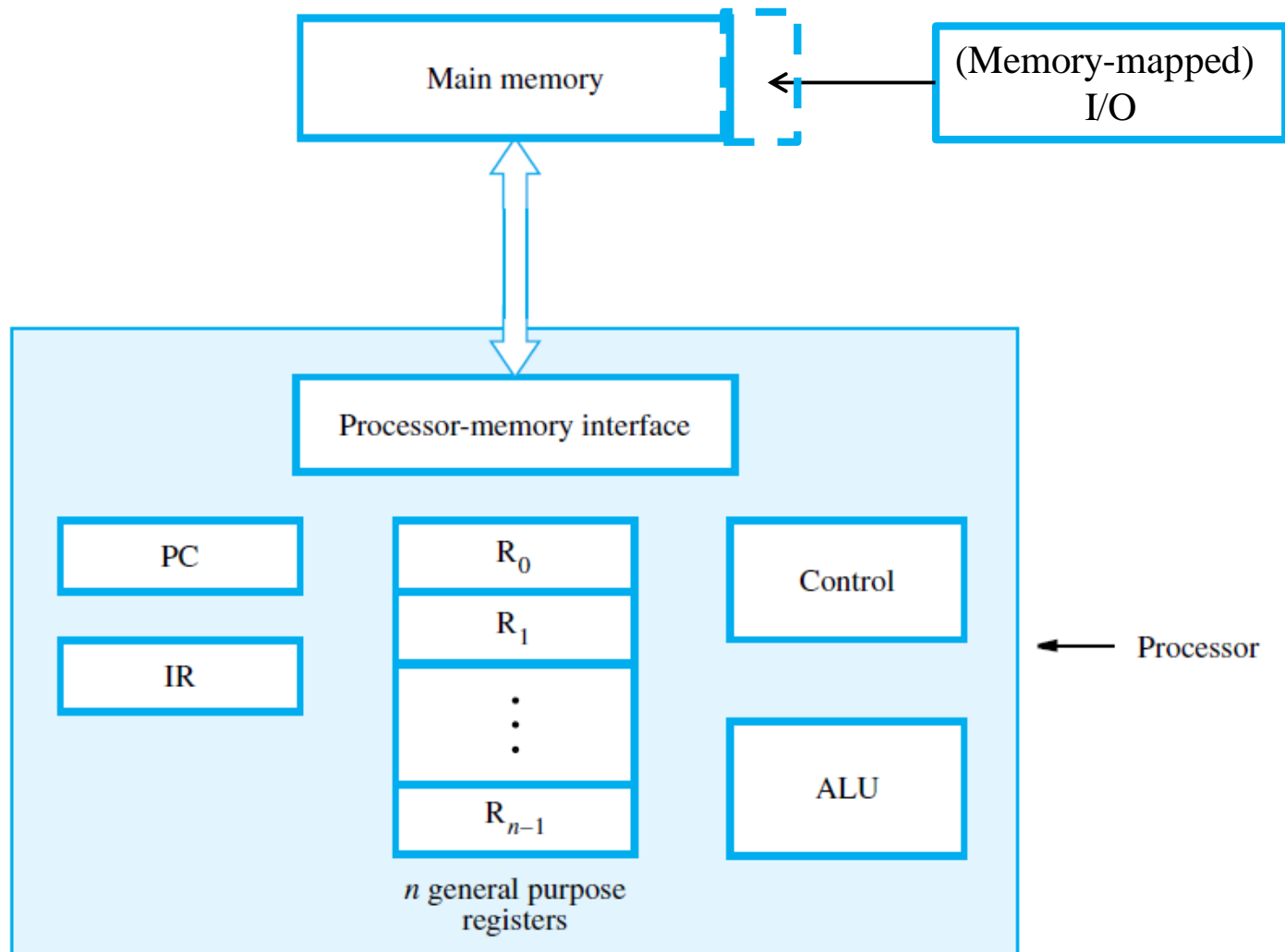


# Complete Datapath

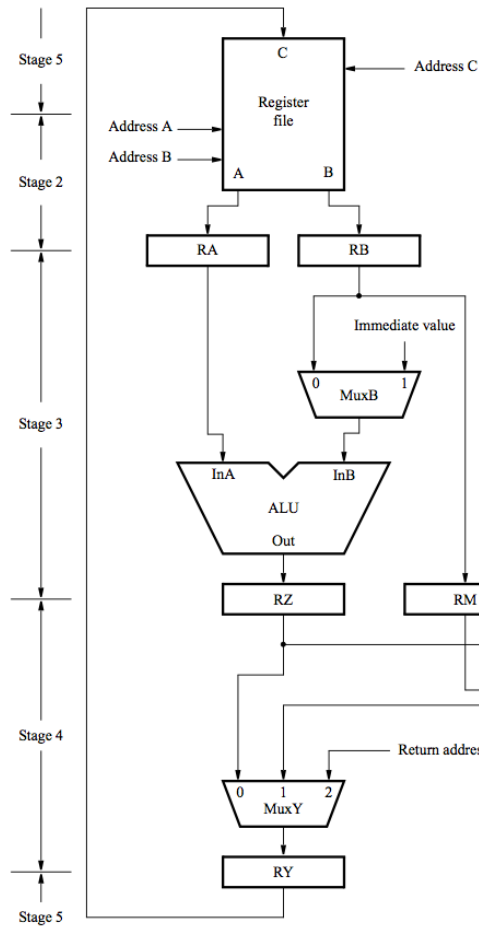


DATA PATH


INSTRUCTION ADDRESS GENERATOR

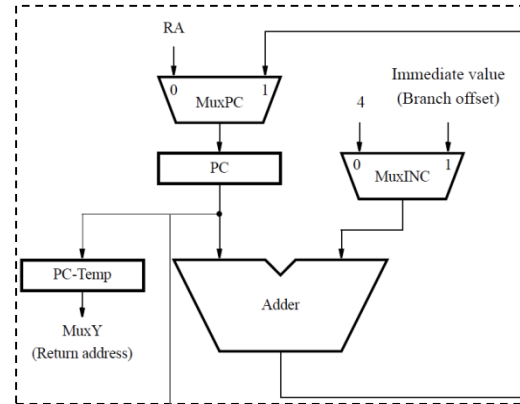

CONTROL UNIT

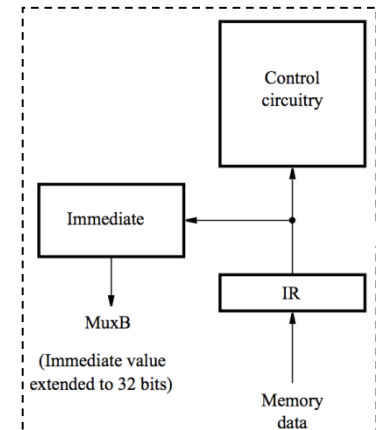


Data address  
Instruction address

 

PROCESSOR-MEMORY INTERFACE

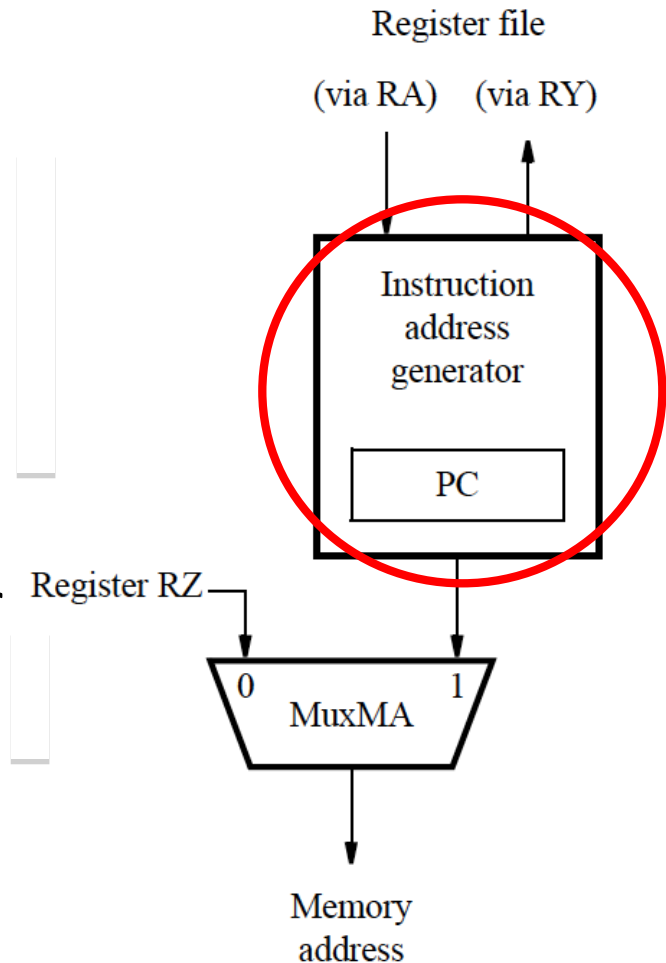
# Memory address generation

- Two kinds:
  - Instruction address (via Input 1)
  - Data address (Via Input 0)
- Instruction address generator updates PC after instruction fetch.
- Also generates (subroutine) branch and subroutine return addresses.
- MuxMA selects RZ when reading or writing data operands.
  - RZ stores the address computed by the ALU.



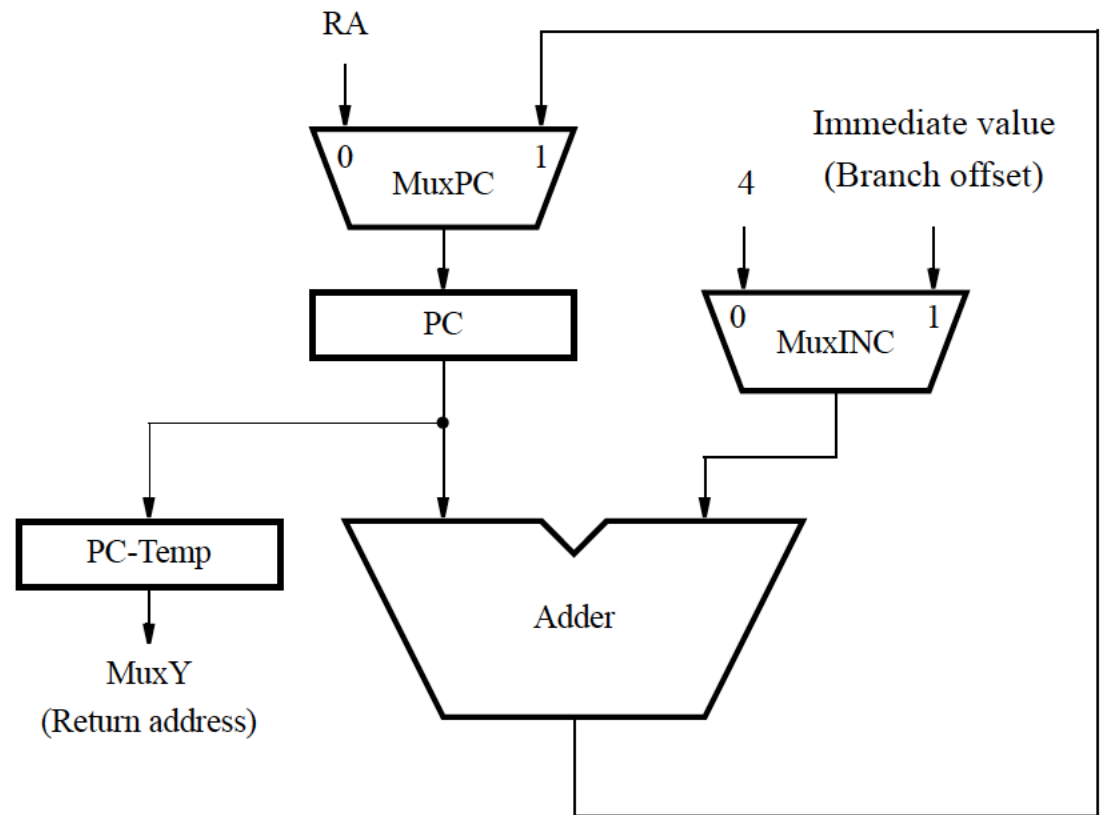
# Instruction address generator

- Connections to RA and RY (via MuxY) are used for subroutine call and return.



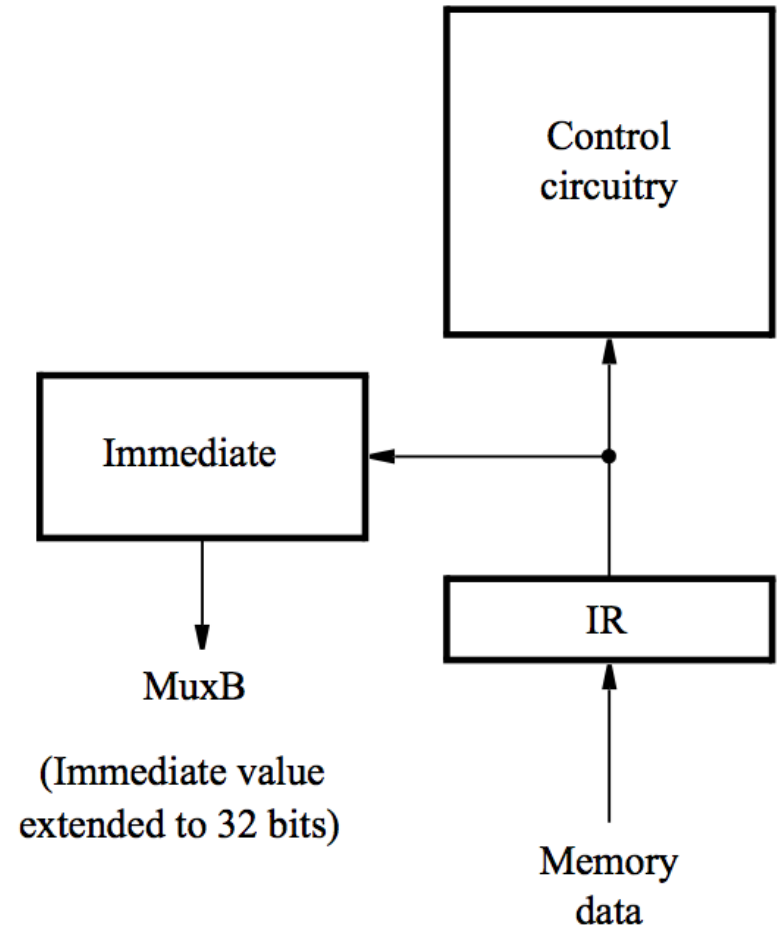
# Processor control section

- When an **instruction** is read, it is **placed in IR**.
- The **control** circuitry **decodes the instruction** and generates the control signals that drive all units (more on this later).
- The **Immediate** block extends the immediate operand to 32 bits as specified in the instruction.




# Instruction Formats (Chapter 5 Processor)


Fig. 5.12

 

(a) Register-operand format

 

(b) Immediate-operand format

 


(c) Call format




# Example: Add R3, R4, R5

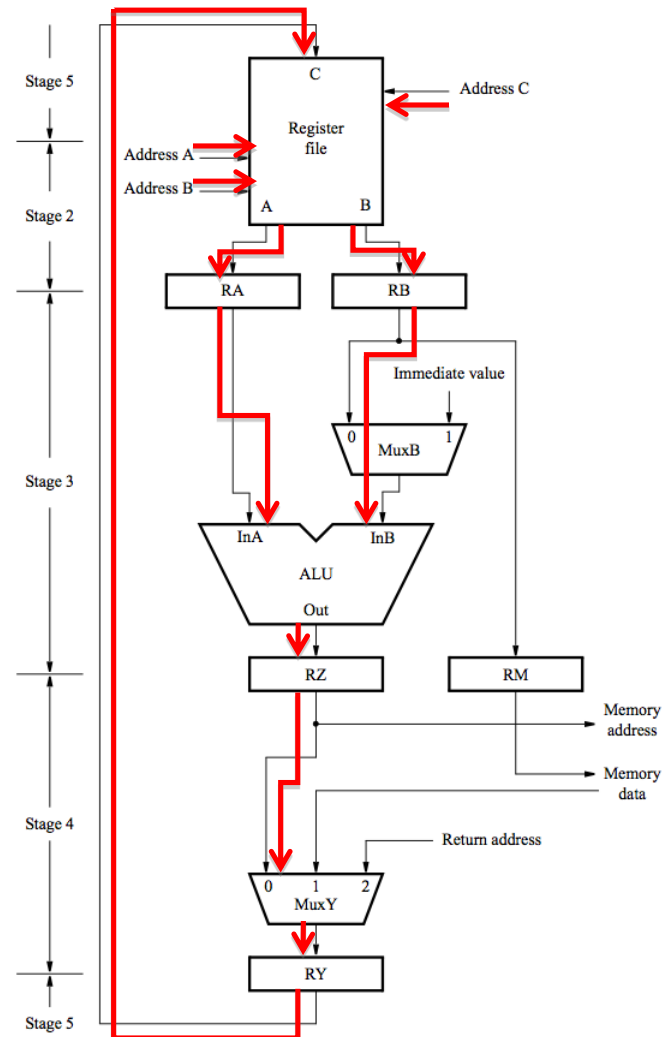1. Memory address  $\leftarrow$  [PC],  
Read memory,  
 $IR \leftarrow$  Memory data,  
 $PC \leftarrow [PC] + 4$
2. Decode instruction,  
 $RA \leftarrow [R4]$ ,  $RB \leftarrow [R5]$
3.  $RZ \leftarrow [RA] + [RB]$
4.  $RY \leftarrow [RZ]$
5.  $R3 \leftarrow [RY]$




# Example: Load R5, X(R7)

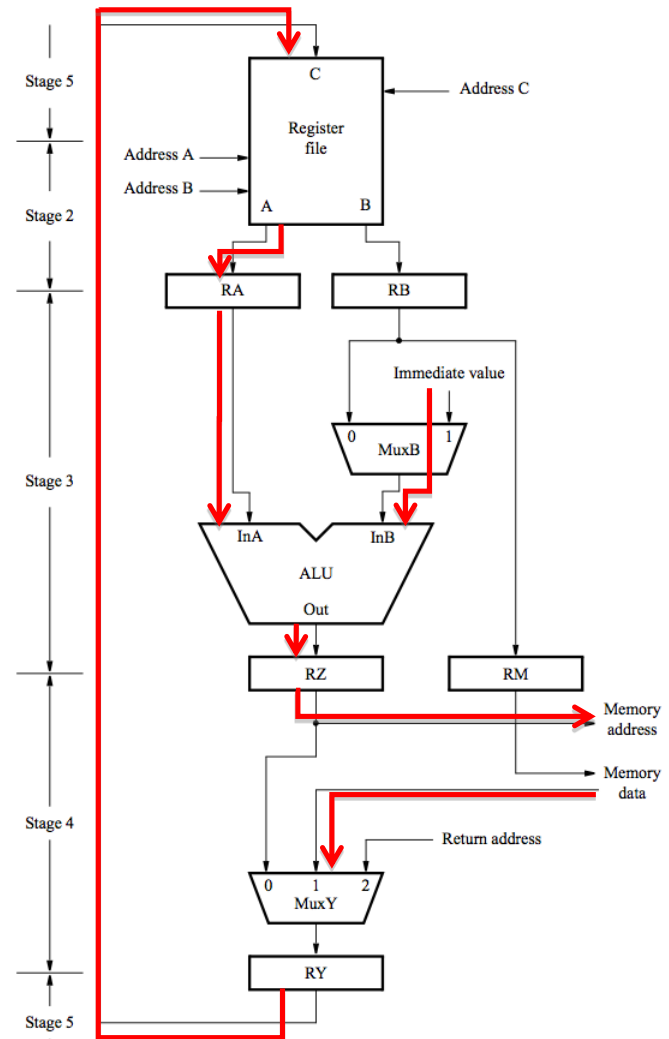1. Memory address  $\leftarrow [PC]$ ,  
Read memory,  
 $IR \leftarrow$  Memory data,  
 $PC \leftarrow [PC] + 4$
2. Decode instruction,  $RA \leftarrow [R7]$
3.  $RZ \leftarrow [RA] + \text{Immediate value } X$
4. Memory address  $\leftarrow [RZ]$ ,  
Read memory,  
 $RY \leftarrow$  Memory data
5.  $R5 \leftarrow [RY]$




# Example: Store R6, X(R8)

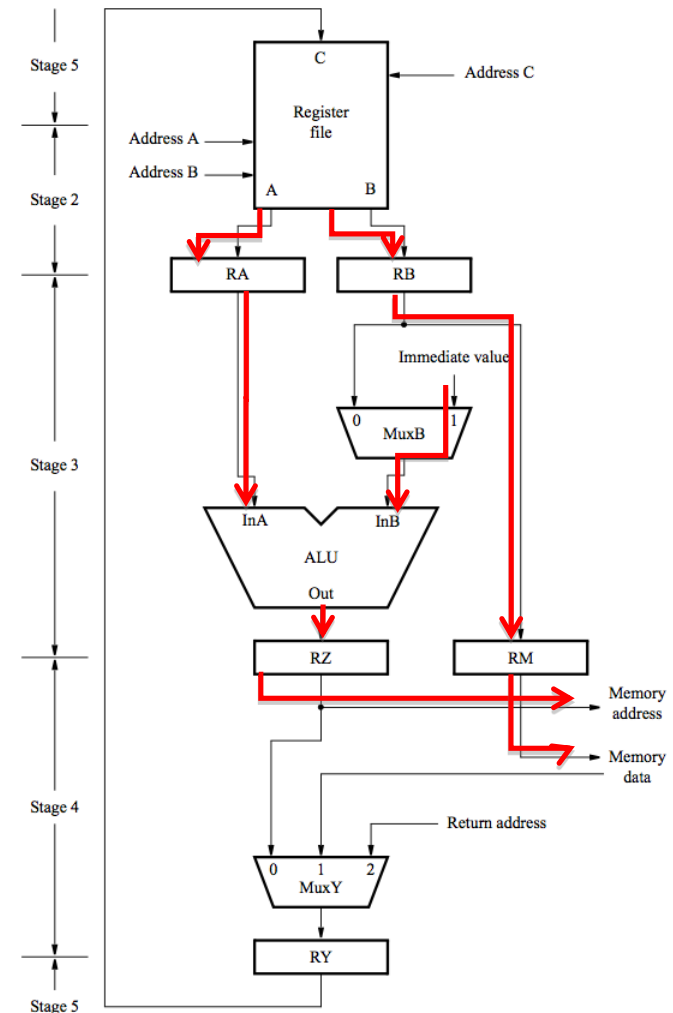1. Memory address  $\leftarrow [PC]$ ,  
Read memory,  
 $IR \leftarrow$  Memory data,  
 $PC \leftarrow [PC] + 4$
2. Decode instruction,  
 $RA \leftarrow [R8]$ ,  $RB \leftarrow [R6]$
3.  $RZ \leftarrow [RA] + \text{Immediate value } X$ ,  
 $RM \leftarrow [RB]$
4. Memory address  $\leftarrow [RZ]$ ,  
Memory data  $\leftarrow [RM]$ ,  
Write memory
5. No action



# Unconditional branch

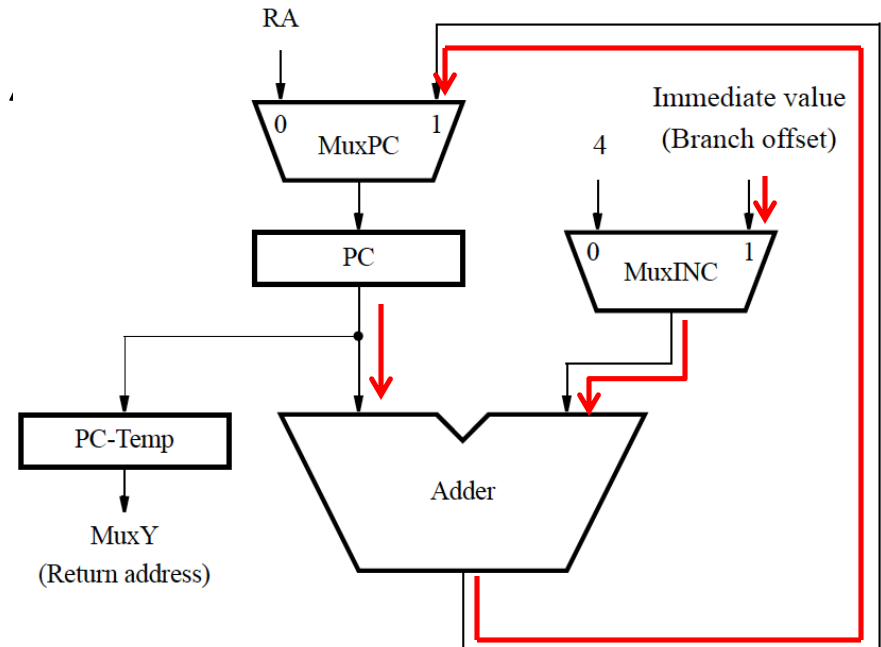1. Memory address  $\leftarrow [PC]$ ,  
Read memory,  
 $IR \leftarrow$  Memory data,  
 $PC \leftarrow [PC] + 4$
2. Decode instruction
3.  $PC \leftarrow [PC] +$  Branch offset
4. No action
5. No action



# Conditional branch:

## Branch\_if\_[R5]=[R6] LOOP

1. Memory address  $\leftarrow$  [PC],  
Read memory,  
IR  $\leftarrow$  Memory data,  
PC  $\leftarrow$  [PC] + 4
2. Decode instruction, RA  $\leftarrow$  [R5], RB  $\leftarrow$  [R6]
3. Compare [RA] to [RB],  
If [RA] = [RB], then PC  $\leftarrow$  [PC] + Branch offset
4. No action
5. No action

Complete the data flow diagram on your own.

# Subroutine call with indirection: Call\_register R9

1. Memory address  $\leftarrow$  [PC],  
Read memory, IR  $\leftarrow$  Memory data,  
PC  $\leftarrow$  [PC] + 4
2. Decode instruction, RA  $\leftarrow$  [R9]
3. PC-Temp  $\leftarrow$  [PC],  
PC  $\leftarrow$  [RA]
4. RY  $\leftarrow$  [PC-Temp]
5. Register LINK  $\leftarrow$  [RY]

Complete the data flow diagram on your own.

# Course Project

- 20% of your **course** grade
- Goals
  - Understand software/hardware interface better by **implementing** a substantial subset of a Reduced Instruction Set Computer (RISC) **instruction set architecture (ISA)**.
  - Understand design parameters that determine the **performance** of hardware design in terms of **timing and utilization** of hardware resources.
  - Learn to **work as a team** to carry out a complex design task requiring task partitioning, effective communication, and cooperation.
  - Produce a report that accurately describes your work according to the best practice in **technical communication**.

# Course Project

- Implement a basic processor with
  - an ISA that strongly resembles a subset of the MIPS architecture
  - some features that are unique to ARM
  - all instructions are 24-bits wide and data is 16-bits wide.
  - pipelining
  - (optional) interrupt capabilities



# Project Timeline

- Consists of 7 steps
- Step 7 – Optional enhancements = Extra credit
- 1- Oct. 29/31 : ALU and Register File (done in lab)
- 2- Nov. 5/7 : Connect ALU and Reg File to datapath & mini report
- 3- Nov. 12/14 : Implement remaining instructions & mini report
- 4- Nov. 19/21 : Add I/O and ARM-like conditional execution & mini report
- 5- Dec. 3/5 : Add pipelining & mini report
- 6- Dec 10/12: Ideally have project done (including extra credit), report started.
- 7- Dec 19 : (Finals week) Present (actually need everything done): Project, Report, Demonstration
- One week before each due date, a handout will be given with more detail on what is due.

# Project Reporting

- Every week you will submit a three-page report describing the portion of the project you worked on that week.
- Concluded with a final report
- More information → Course Documents/  
**Project** section of Blackboard.

# Project Grading

- 500 points → 20% of course grade (+150)
- Parts 2-4: 50 Pts each
- Part 5: 100 Pts
- Final Part: 200 Pts
  - 100 Pts: Report
  - 50 Pts: Presentation
  - 50 Pts: Demonstration
- Individual: 50 Pts
  - Our assessment of each member's contribution (5 Pts/week)
  - Peer evaluation form (25 Pts)
- Bonus: Up to 150 Pts – Depends on the difficulty and success of the extras

# Upcoming...

- Homework 4 – Chapter A
  - Due Friday, Oct. 25<sup>th</sup>
- Quiz 4 – Chapter A (A.1-A.5)
  - Monday, Oct. 28<sup>th</sup> (15 min)
- Midterm – Chapter 1, 2, 3
  - Monday, Nov. 4<sup>th</sup> (50 min)
- Test 2 – Chapters A & 5
  - Monday, Nov. 11<sup>th</sup> (50 min)